

4.1-4.2: Instruction-Set Architecture & Logic design

周百川 2024.10.16


01 Instruction-Set Architecture(ISA)

Y86-64:

Similar to x86-64 but simpler;

Between CISC and RISC

Programmer-Visible State

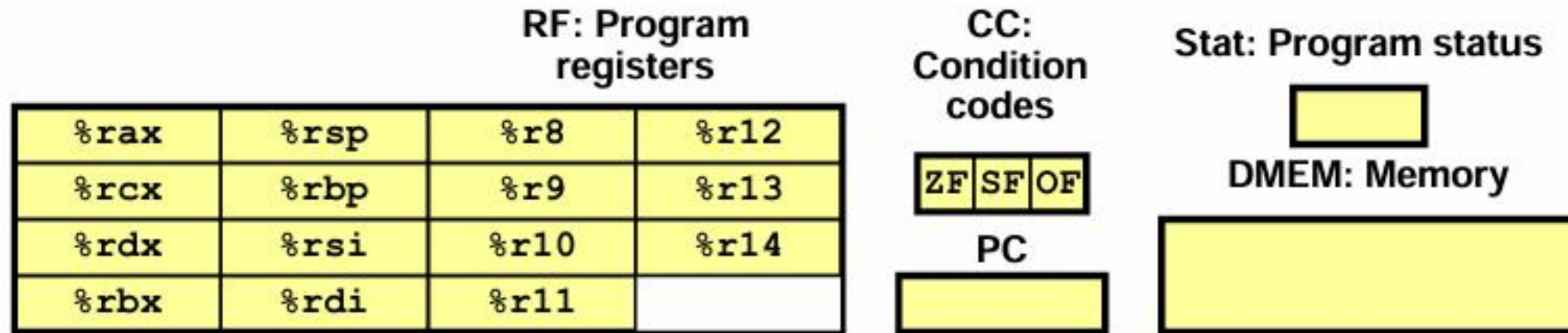

Registers: 15 registers, no %r15

Conditional Codes: Zero/Negative/Overflow

Stat: AOK/HLT/ADR/INS

Memory: a big array

Instructions

- **halt**: 0 0, suspend instruction execution and set Stat to HLT
- **nop**: 1 0, no operation

halt

0	0
---	---

nop

1	0
---	---

Instructions

- Moves

Code: 2 X(0-6) rA rB

rrmovq is a 'unconditional move'

rrmovq

2	0
---	---

cmovne

2	4
---	---

cmovle

2	1
---	---

cmovge

2	5
---	---

cmovl

2	2
---	---

cmovg

2	6
---	---

cmovbe

2	3
---	---

rrmovq **rA**, **rB**

2	0	rA	rB
---	---	-----------	-----------

cmovXX **rA**, **rB**

2	fn	rA	rB
---	-----------	-----------	-----------

Instructions

- Moves

Code: X 0 rA rB
(V/D)(8bytes)

`rrmovq rA, rB`

2	0	rA	rB
---	---	----	----

`irmovq V, rB`

3	0	F	rB	V
---	---	---	----	---

`rmmovq rA, D(rB)`

4	0	rA	rB	D
---	---	----	----	---

`mrmovq D(rB), rA`

5	0	rA	rB	D
---	---	----	----	---

register ID:

0xF means no register
should be accessed

Number	Register name	Number	Register name
0	%rax	8	%r8
1	%rcx	9	%r9
2	%rdx	A	%r10
3	%rbx	B	%r11
4	%rsp	C	%r12
5	%rbp	D	%r13
6	%rsi	E	%r14
7	%rdi	F	No register

Instructions

- Operations

Code: 6 X(0-3) rA rB

*can only operate registers

addq

6	0
---	---

subq

6	1
---	---

andq

6	2
---	---

xorq

6	3
---	---

OPq **rA**, **rB**

6	fn	rA	rB
---	-----------	-----------	-----------

Instructions

- Branches

Code: 7 X(0-6) Dest(8 bytes)

jmp	7	0	jne	7	4
jle	7	1	jge	7	5
j1	7	2	jg	7	6
je	7	3			

jXX Dest

7	fn	Dest
---	----	------

Instructions

`call` and `ret`,
`pushq` and `popq`

Code:

`call:8 0 Dest(8 bytes)`

`ret:9 0`

`pushq:A 0 rA F`

`popq:B 0 rA F`

`call Dest`

8	0	Dest
---	---	------

`ret`

9	0
---	---

`pushq rA`

A	0	rA	F
---	---	----	---

`popq rA`

B	0	rA	F
---	---	----	---

Exceptions

Value	Name	Meaning
1	AOK	Normal operation
2	HLT	halt instruction encountered
3	ADR	Invalid address encountered
4	INS	Invalid instruction encountered

02 Logic Design

HCL:Hardware Control Language




Can be translate into Verilog and further a working microprocessor

Logic Gates


AND: &&

OR: ||

NOT: !

   


Combinational Circuits

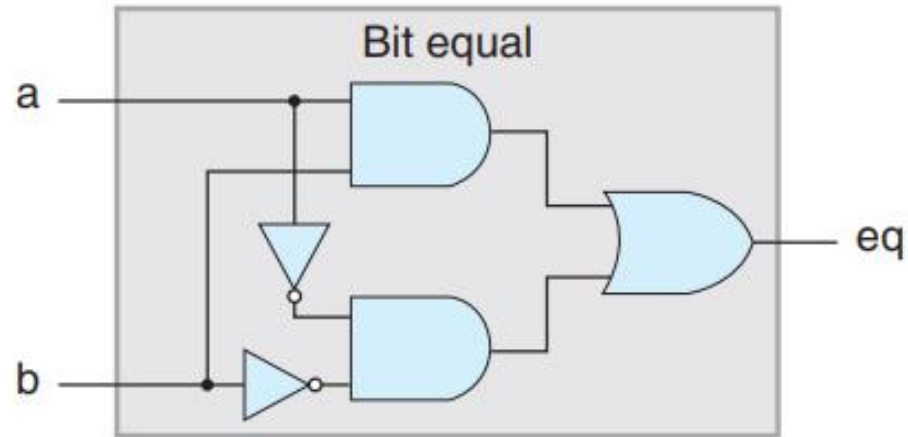

bit equal


```
bool eq = (a && b) || (!a && !b)
```

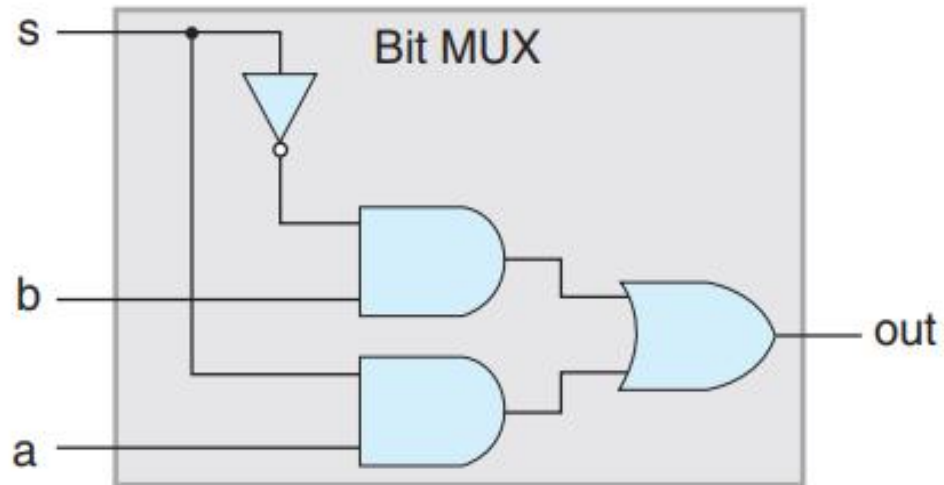


bit MUX

```
bool out = (s && b) || (!s && a)
```

Combinational Circuits

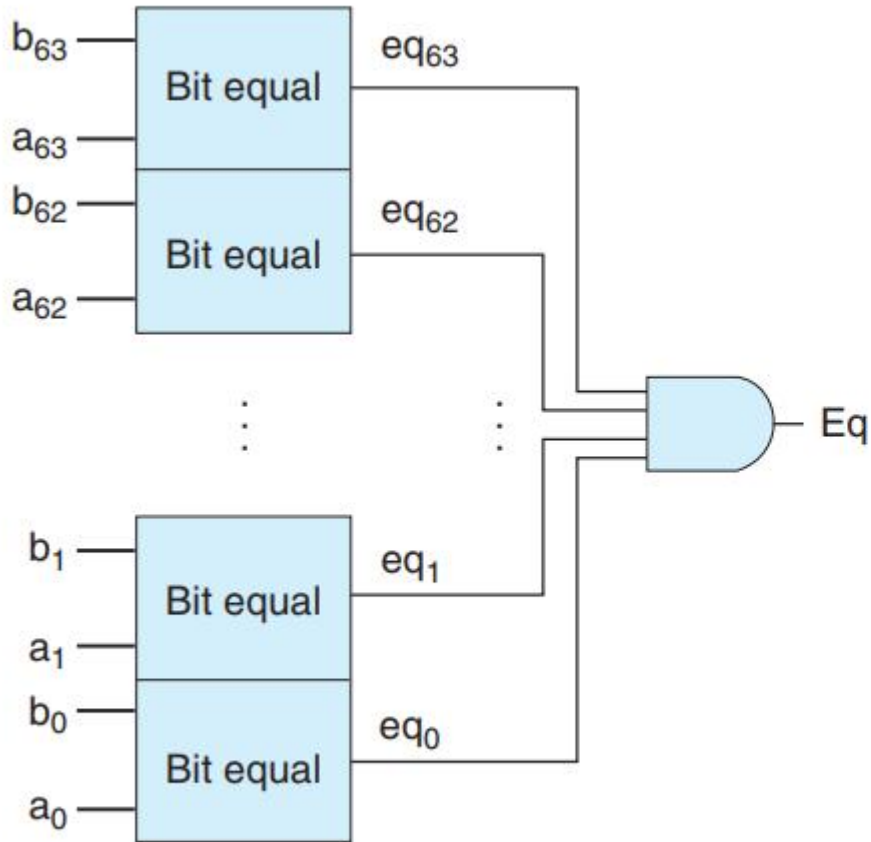

(a) Bit-level implementation

 


(b) Word-level abstraction


word equal

bool Eq = (A == B)

Combinational Circuits

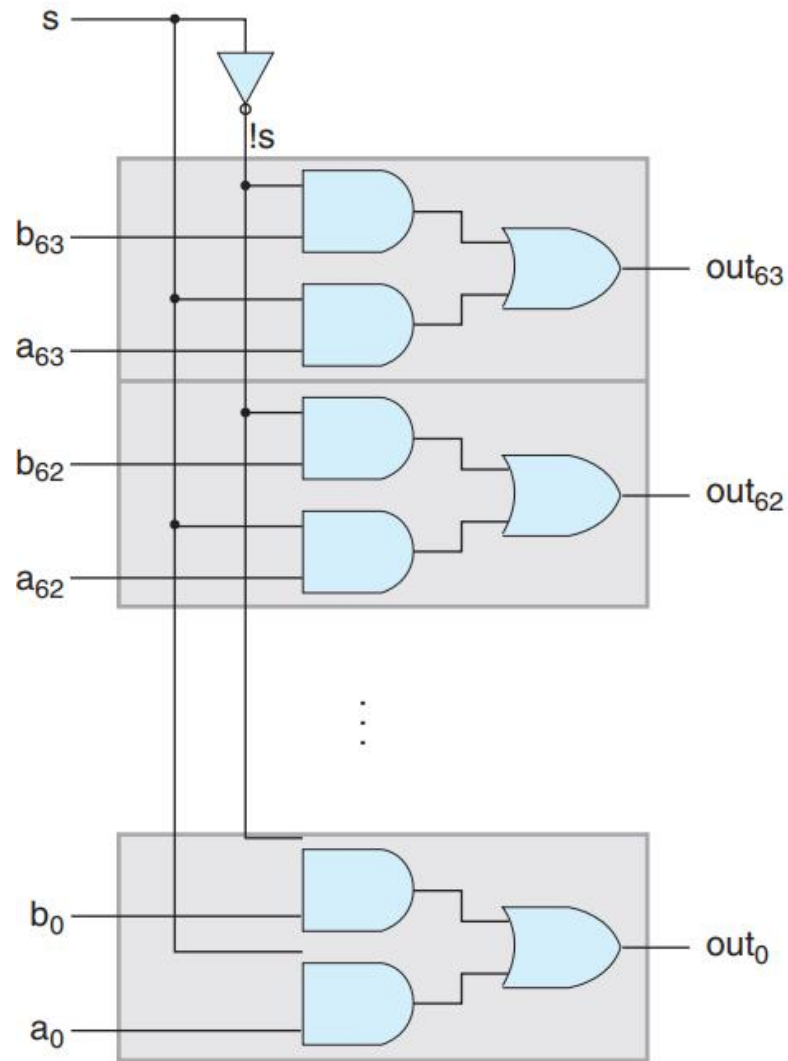

(a) Bit-level implementation

 


(b) Word-level abstraction

word MUX

```
word Out = [  
    s: A;  
    1: B;  
];
```

```
int Out = [  
    s : A;  
    1 : B;  
];
```


Combinational Circuits

 

Four-way MUX


```
word Out4 = [  
    !s1 && !s0 : A; # 00  
    !s1       : B; # 01  
    !s0       : C; # 10  
    1         : D; # 11  
];
```


Combinational Circuits

 


```
word Min3 = [  
    A <= B && A <= C : A;  
    B <= A && B <= C : B;  
    1                  : C;  
];
```

Arithmetic/logic unit (ALU)

 



Register

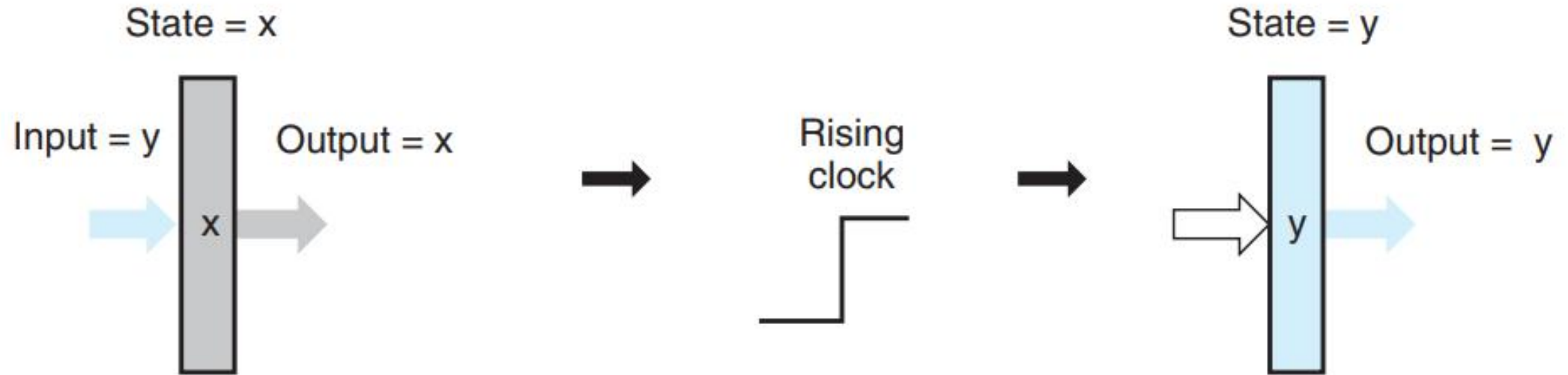

hardware registers != program registers

Register file

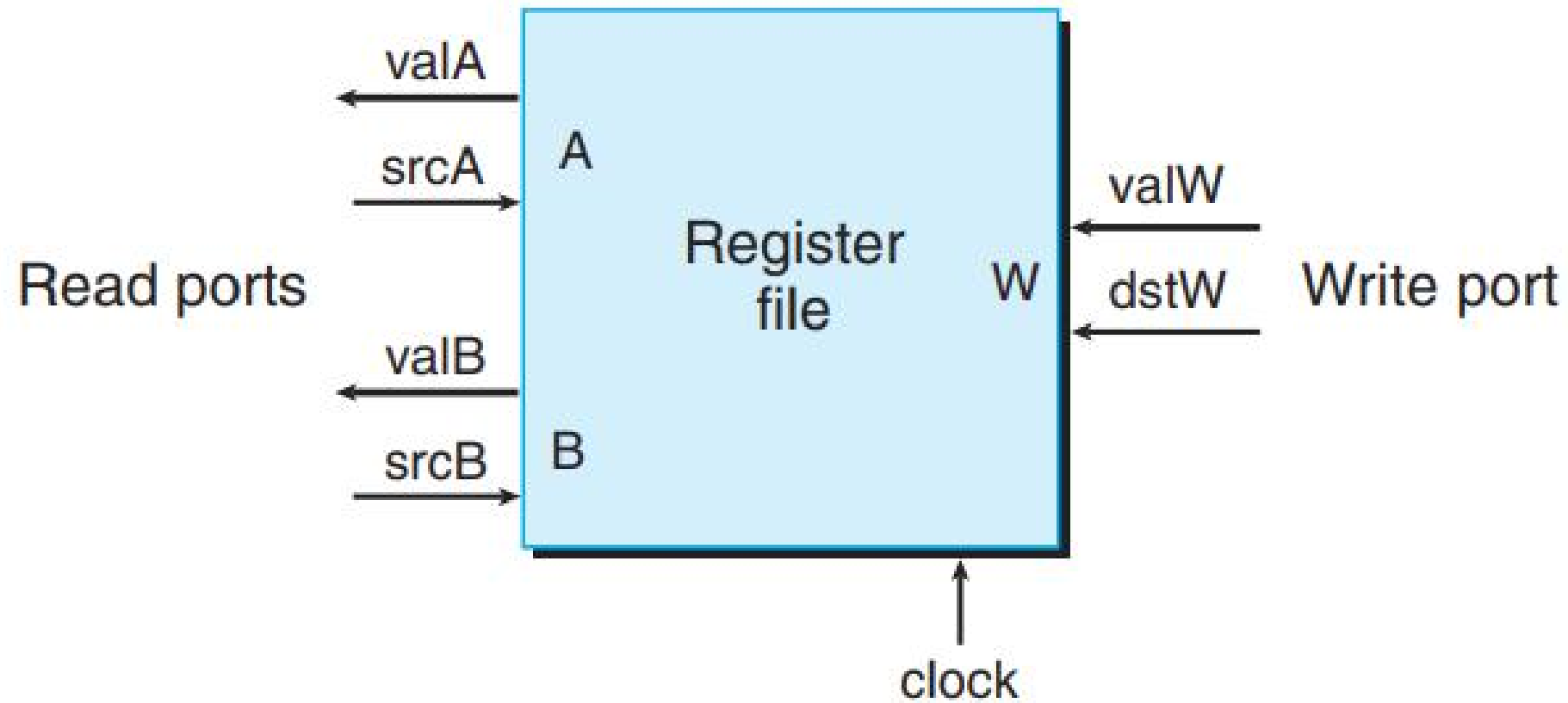

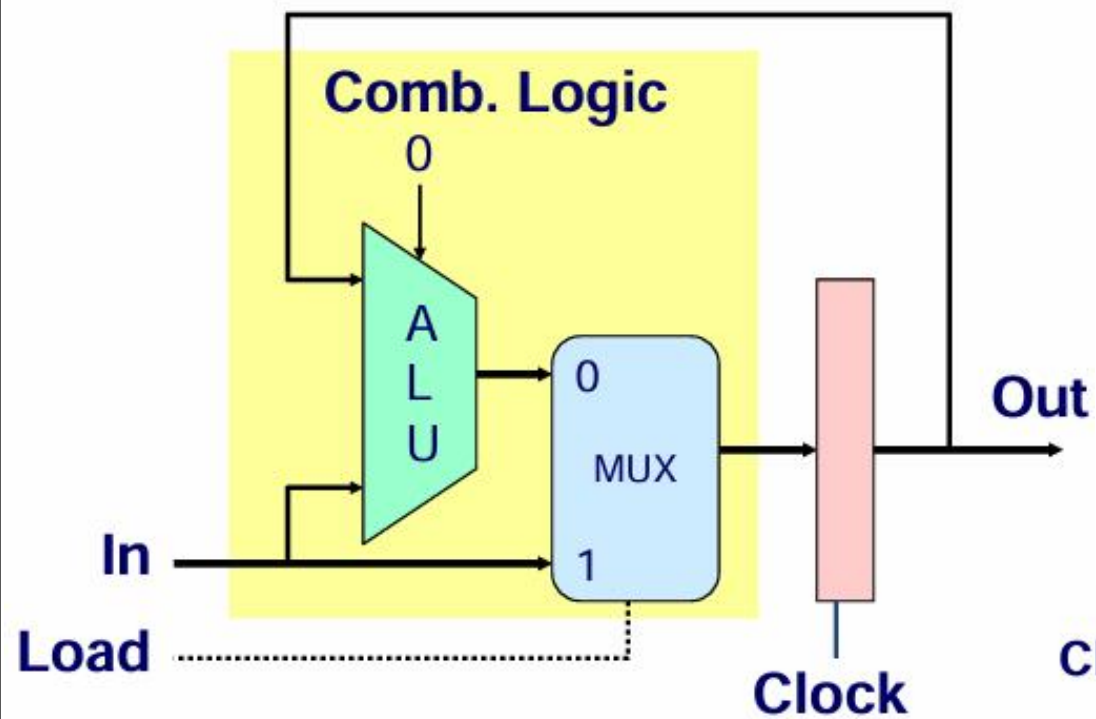

- Accumulator circuit
- Load or accumulate on each cycle

